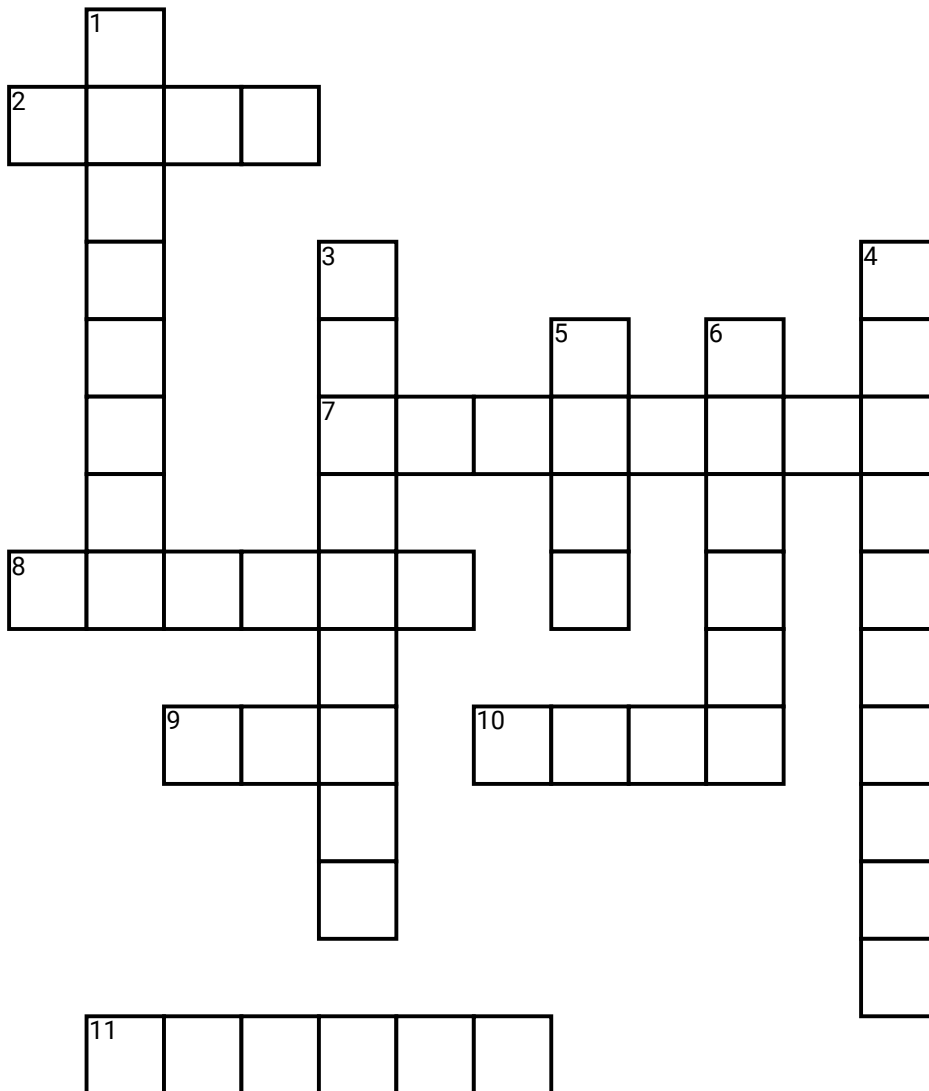


Name: \_\_\_\_\_

Date: \_\_\_\_\_

# Circuits



## Across

- 2.** A circuit forms this.
- 7.** Electricity leaves this end of the battery.
- 8.** This type of circuit has more than 1 bulb.
- 9.** A bulb must be this to know that the circuit works.
- 10.** Electricity travels through this to light the bulb.
- 11.** Another word for battery.

## Down

- 1.** Electricity travels to this end of the battery.
- 3.** All parts must be \_\_\_\_\_ for the circuit to work.
- 4.** This type of energy passes through a circuit.
- 5.** In a series circuit, electricity only has one of these.
- 6.** This type of circuit only has 1 bulb.