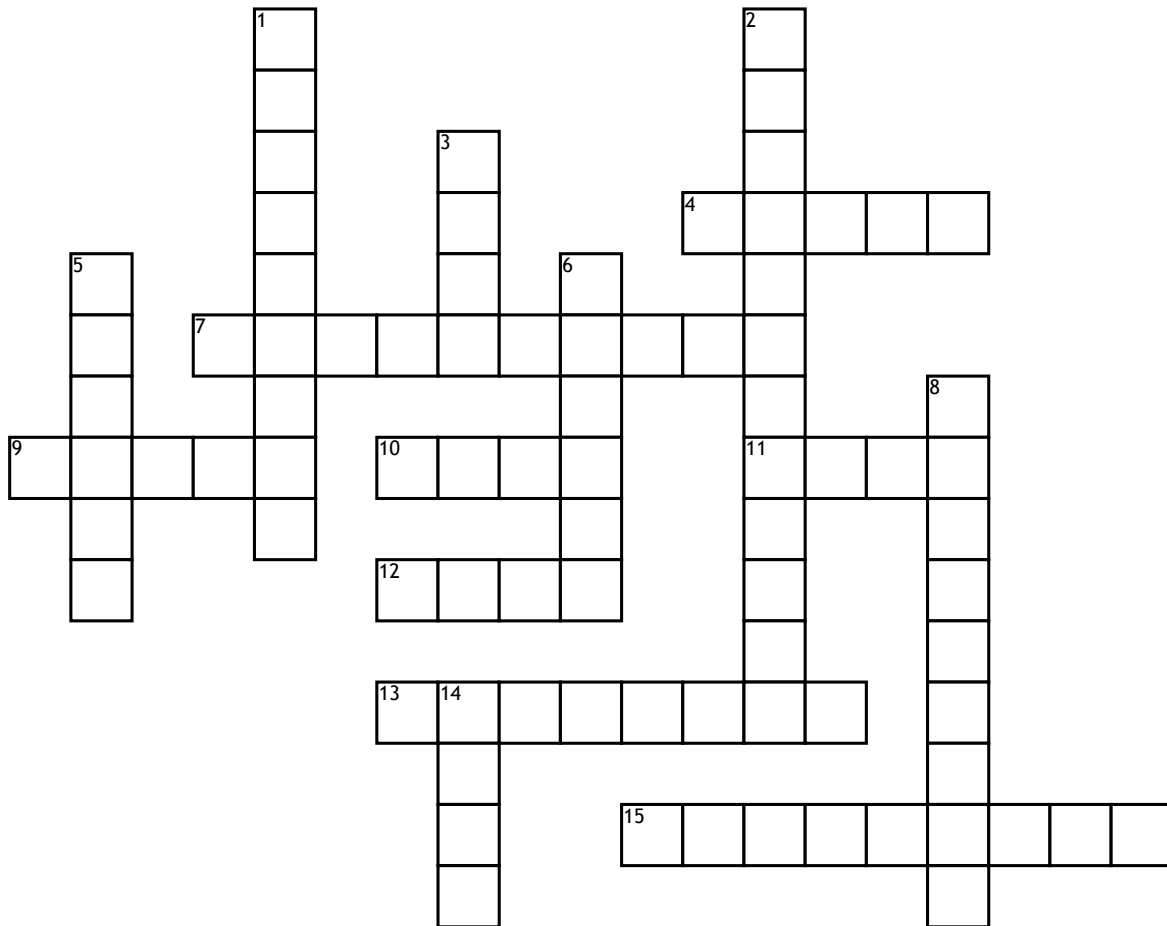


Electricity Revision



Across

4. The _____ wire is green and yellow. (5)
 7. potential difference = current x _____ (10)
 9. A _____ only allows current to flow in one direction. (5)
 10. The _____ wire is brown. (4)
 11. charge = current x _____ (4)

12. _____ Law says that current is proportional to pd.
 13. Charge is measured in _____. (8)
 15. Mains electricity has a _____ of 50Hz. (10)

Down

1. Potential difference is measured using a _____. (9)
 2. The IV graph for a _____ is an S shape. (8,4)

3. Current is measure in _____. (4)
 5. In a _____ the current is the same everywhere. (6)
 6. In parallel the pd across each branch is the _____ the pd of the battery. (4,2)
 8. The resitance of an LDR _____ when light intensity increases. (9)
 14. Resistance is measured in _____. (4)