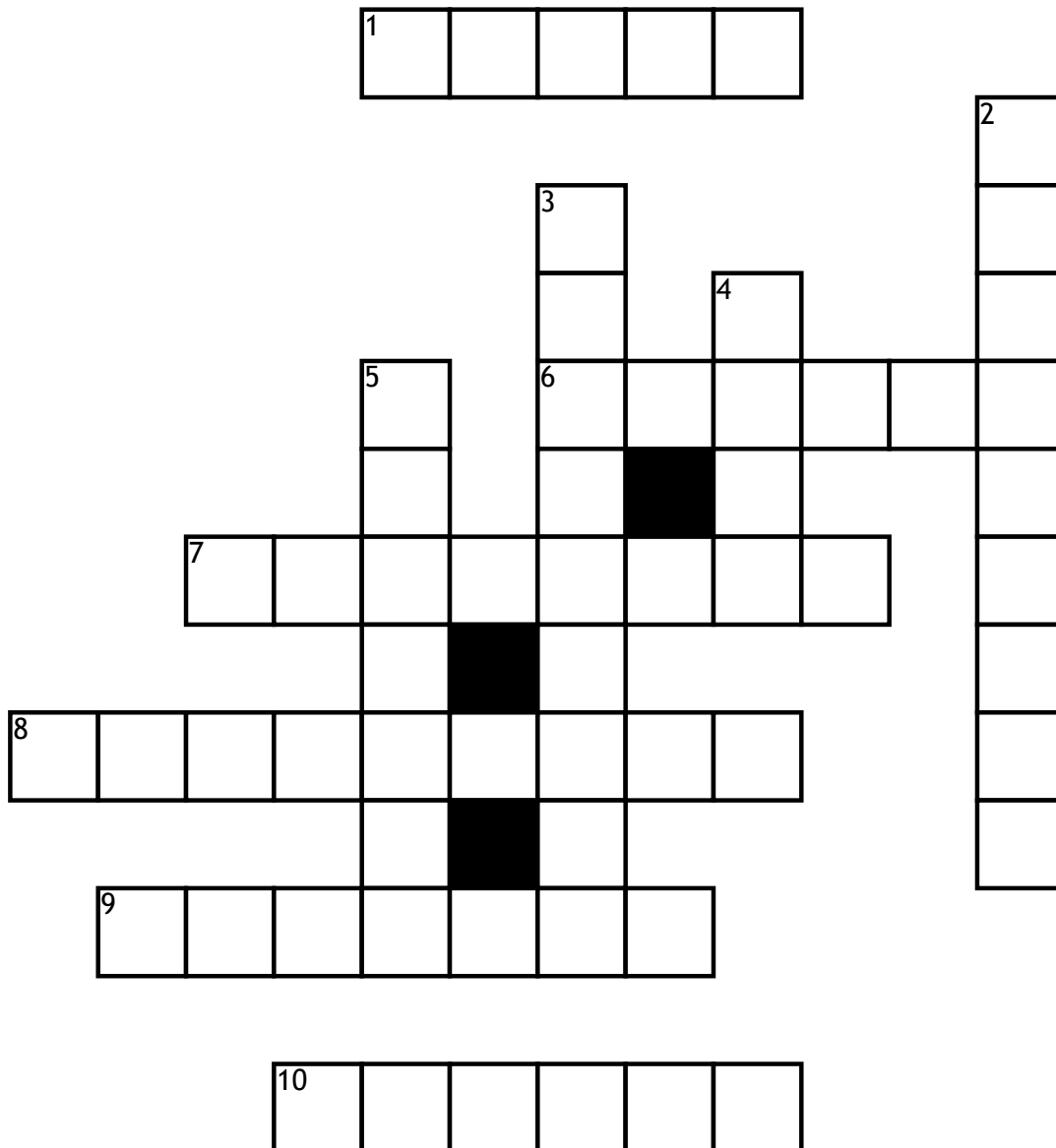


Name: \_\_\_\_\_

Date: \_\_\_\_\_

# Energy



## Across

1. Produces motion in a circuit
6. Turns a circuit on and off
7. a circuit with two paths
8. A material in which electricity travels through
9. A source of energy used in a circuit
10. a circuit with only on path

## Down

2. produces light in a circuit
3. A material in which electricity can not travel through
4. This is a component in a circuit that helps energy travel
5. the path through which electricity flows