
Name: _____ Date: ____

Science Vocabulary Energy

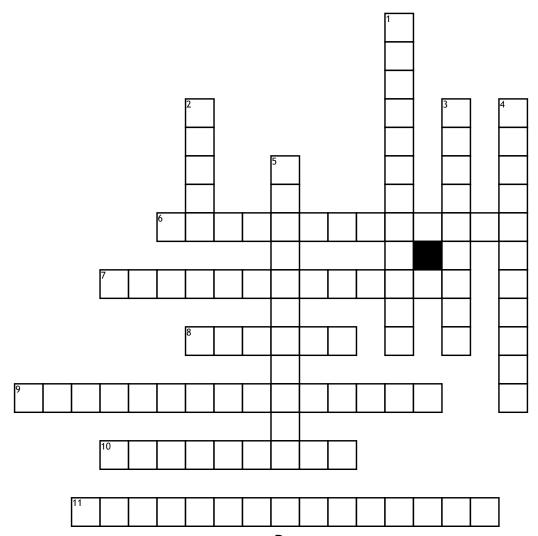

<u>Across</u>

- **6.** A complete circuit through which electricity flows
- **7.** A circuit that has only one pathway for current to flow
- **8.** The ability to do work.
- **9.** The flow of electricity through a conductor **10.** A material that prevents the flow of electricity
- **11.** A circuit that has two or more pathways for current to flow.

<u>Down</u>

- 1. When an electric current doesn't travel it's intended path
- **2.** A source of electricity; also known as a battery.
- **3.** A substance, commonly a metal such as copper or aluminum, through which electricity will flow.
- **4.** Energy that flows through circuits and can produce light, heat, motion, and sound.
- **5.** An incomplete circuit through which electricity will not flow.

Word Bank

Electricity conductor
Parallel Circuit Insulator
Short circuit Closed circuit

D-cell Open circuit Energy Electric current Series Circuit